



VIT[®]
Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)

Task – 5

Antenna and Microwave Lab

NAME: - Rahil Alawat

REG NO.: - 21BEC2427

SLOT - E2

SUBMITTED TO: - Prof. Poonkuzhali R

Experiment - S card I

Aim → Design an amplifier for the max gain at 4.0 GHz using single-stub matching section. Calculate and plot the z/p return loss and the gain from 3 to 5 GHz. The GaAs FET has following S-parameters ($Z_0 = 50 \Omega$)

f (GHz)	S_{11}	S_{21}	S_{12}	S_{22}
3.0	$0.80 \angle -89^\circ$	$2.86 \angle 99^\circ$	$0.03 \angle 56^\circ$	$0.76 \angle -41^\circ$
4.0	$0.72 \angle -116^\circ$	$2.60 \angle 76^\circ$	$0.02 \angle 57^\circ$	$0.73 \angle -54^\circ$
5.0	$0.66 \angle -142^\circ$	$2.39 \angle 54^\circ$	$0.03 \angle 62^\circ$	$0.72 \angle -68^\circ$

Substrate Specification →

$$\epsilon_r = 4.4$$

$$\tan \delta = 0.0001$$


$$H = 1.6 \text{ mm}$$

$$T = 0.05 \text{ mm}$$

theoretical gain :-


$$G_T = 16.7 \text{ dB}$$

model graph →

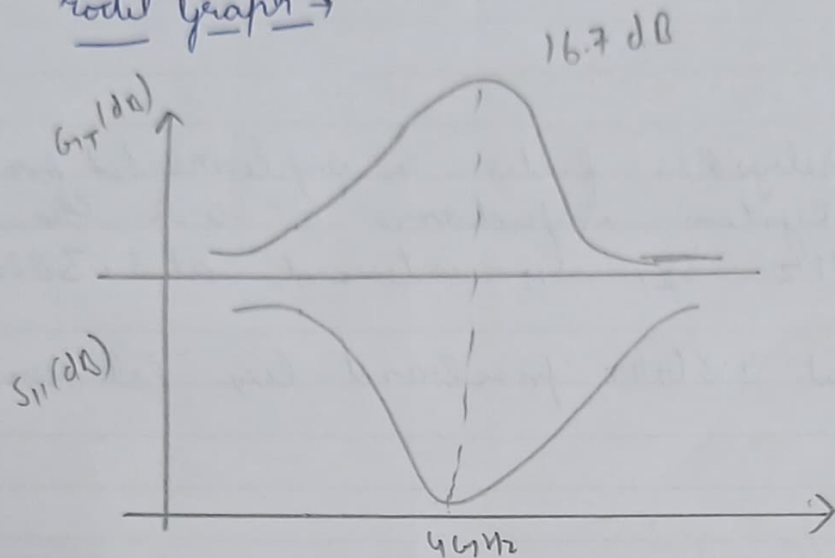

$$\Gamma_S = \frac{B_1 \pm \sqrt{B_1^2 - 4|C_1|^2}}{2C_1} = 0.872 \angle 123^\circ$$

$$\Gamma_L = \frac{B_2 \pm \sqrt{B_2^2 - 4|C_2|^2}}{2C_2} = 0.876 \angle 61^\circ$$

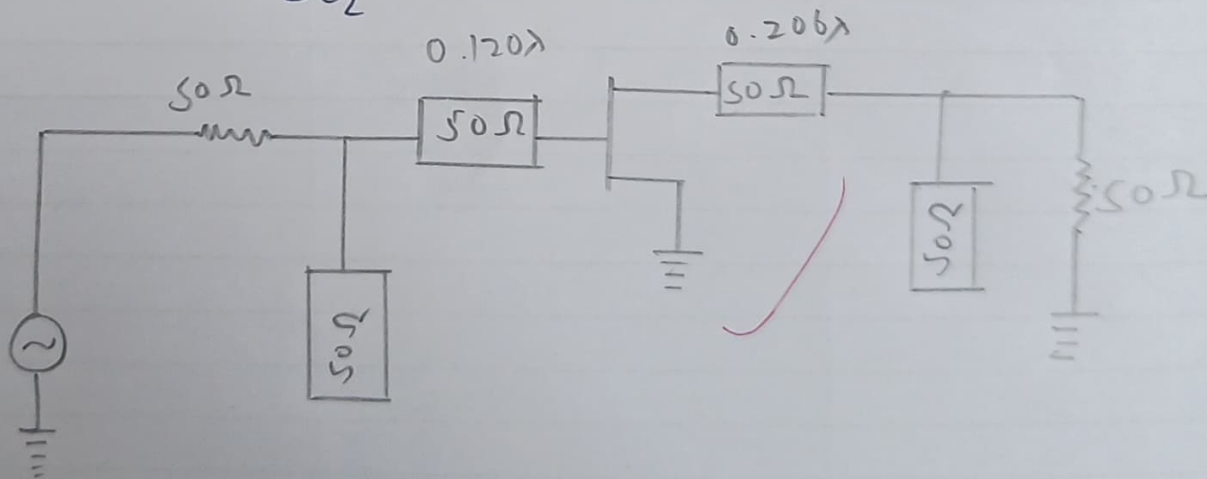

Z		Electrical length (βl)	W (mm)	l (mm)
$Z_0 = 50 \Omega$	0.120λ	$0.120 \times 360^\circ = 43.2$	3.02825	4.87918
$Z_0 = 50 \Omega$	0.120λ	$0.206 \times 360^\circ = 74.16$	3.02825	18.37592

Tabular Column →

Frequency (cps)	0.0 (1.5(1,1)1)	0.8 (K ₁ T(1,1)1)
1	1.5834	9.6184
2.5	0.7377	7.2929
2	0.11289	5.4817
2.5	-0.37491	4.4417
3	-0.82290	4.6108
3.5	-1.474	7.1828
⇒ 4	-33.652	16.524
4.5	-0.29542	-11.011
5	-0.641335	-22.537
5.5	-0.24226	-14
6.0	-0.71228	-7.2525
6.5	-0.47627	-2.21
7	-0.34567	2.4637

Teacher's Signature _____

Inference →

- ① Min^m return loss is obtained at 4.6142 as $S_{11}(dB) = -2.5$ in the simulation.
- ② max gain of -16.534 is obtained at 4.6142 and the same as verified with theoretical value of -16.534.
- ③ Input matching & O/P matching are designed using smith chart & the same are included in the simulation.

✓
10/10/24

21 DEC 24 27

Exts Part I

$$l = 0.0206\lambda$$

Rohit Navat

$$Q_3 = 0.2081$$

$$C_3 = 3.2$$

$$0.2081$$

$$Q_5 = 0.21$$


towards
load

10/10/24

$$d = 0.1201$$

$$0.4161$$

$g = 0$
for
D.L
Stub

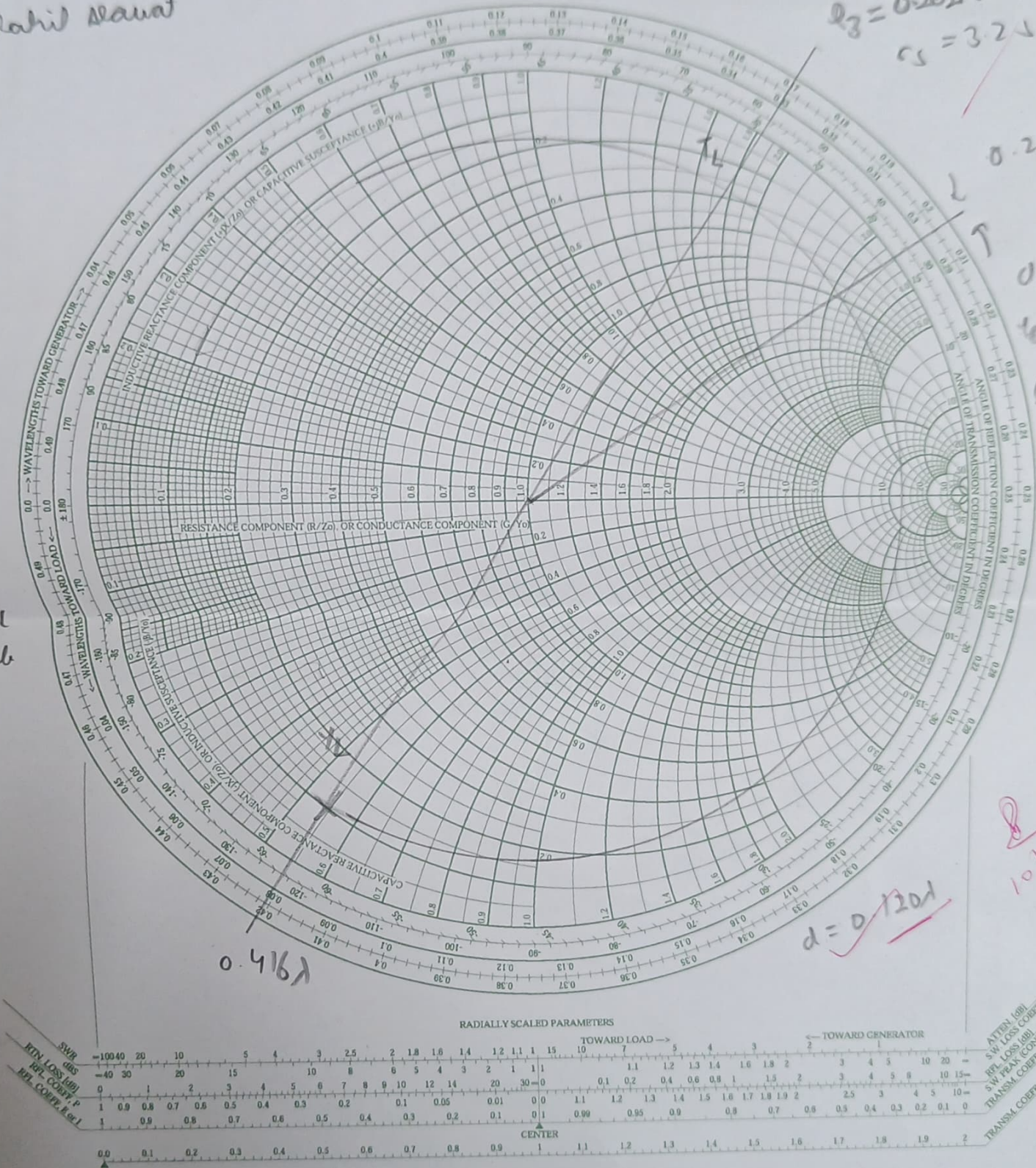


Smith Chart

$\beta = 0.206\lambda$

218EC2427

Rahul Alawat

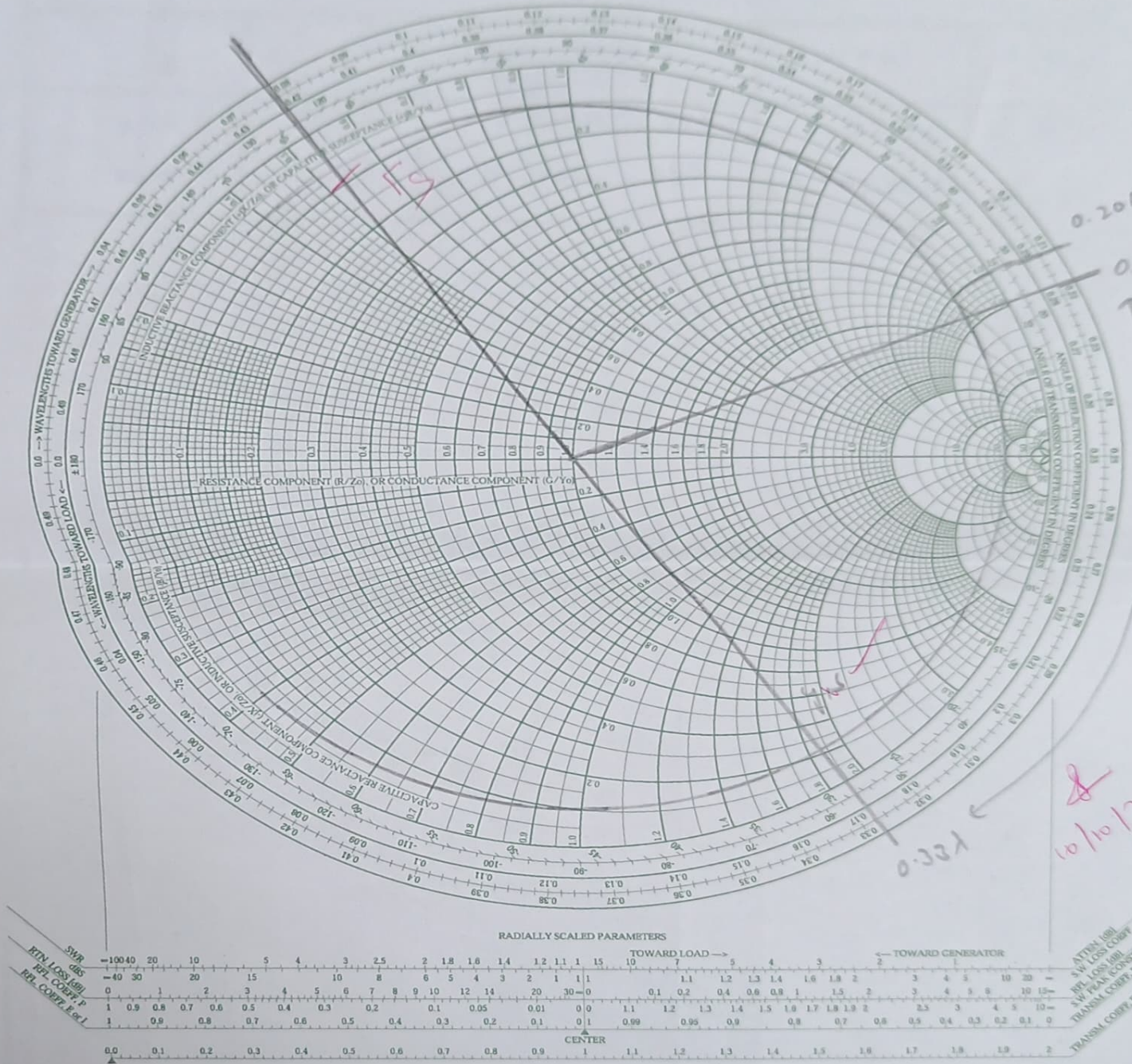

Smith Chart

218EC2427

Scale

1 - mm / unit = 0.05 cm

2 - cm / unit = 0.06 cm

